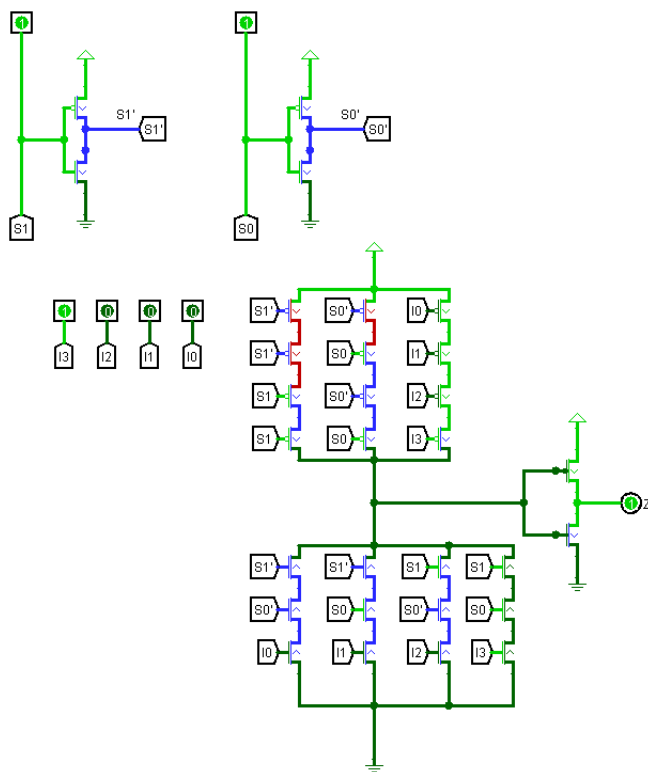


# DD Lab 6 Assignment

Sai Kartik  
2020A3PS0435P

October 16, 2021

## 1 4:1 Mux using CMOS logic



## 2 4:1 Mux using TG and NOT gates

